



# TN90003

## The Qrr of a MOSFET: its importance in motor-control circuit designs

Rev. 1.0 — 21 July 2020

technical note

### Document information

Information	Content
Keywords	MOSFET, reverse recovery charge, Qrr
Abstract	When choosing a MOSFET for a motor-control application, design engineers tend to first study the device's on-resistance characteristic, since this parameter has the greatest effect on the MOSFET's ability to provide sufficient current to the motor without generating excessive heat caused by conduction losses. Some other aspects of the MOSFET's operation also have a marked effect on thermal performance, and attention paid to these factors can offer worthwhile rewards in improved motor-drive design features..

## 1. Introduction

Motor-drive circuits generally switch at lower frequency (typically 20 kHz - 40 kHz) than switch mode power supplies (SMPS, normally 100+ kHz). This often induces designers to ignore the thermal contribution from MOSFET dynamic switching losses attributable to parameters such as input and output capacitance, since they are assumed to be much smaller than the effect of conduction losses attributable to on-resistance.

In motor-control applications, however, in which the motor and controller are often physically connected by wires, design engineers are increasingly taking account of EMC (Electro-Magnetic Compliance) at the component selection phase. The non-ideal switching behavior of a MOSFET can have a marked effect on electro-magnetic emissions: problems caused by these emissions might only become apparent at the qualification phase of the design project.


Furthermore, the efficiency of the motor drive does not have an important effect on system efficiency since motors are inherently less efficient than motor drives: 80-85% efficiency is typical for a motor, whereas a drive circuit's efficiency often exceeds 95%.

MOSFET losses in the drive circuit do however greatly affect the operating temperature of the control circuit's PCB (Printed-Circuit Board), and since the MOSFET's on-resistance increases as temperature rises, then excessive heating must be avoided through good design and component selection. As OEMs (Original Equipment Manufacturer) strive to meet consumer demand for smaller, more powerful products such as hand-held power tools and domestic appliances, MOSFETs which generate less waste heat can enable the designer to achieve reductions in size, weight and cost as well as to extend battery run-times.
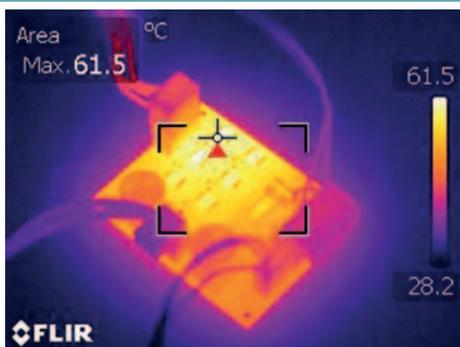
## 2. Adding a gate resistor

To reduce electro-magnetic emissions in motor-control applications, it is common practice to add a resistor in series with the MOSFET's gate. When combined with the MOSFET's capacitive gate, the resistor makes a low-pass filter which helps to reduce the switching speed of the MOSFET. This can be an effective means of reducing high-frequency harmonics, which contribute to the circuit's electro-magnetic emissions. But designers must be careful not to add too much resistance at the MOSFET's gate, since reducing the switching speed extends the time during which the MOSFET operates in linear mode, causing it to dissipate more waste energy.

The heating effect of adding a 47  $\Omega$  gate resistor can easily be observed with a thermal camera, as shown in [Fig. 1](#) and [2](#).



gate resistor = 0  $\Omega$ ; load current = 3 A

**Fig. 1. MOSFET temperature = 61.5 °C**




gate resistor = 47  $\Omega$ ; load current = 3 A

**Fig. 2. MOSFET temperature = 65.6 °C**


### 3. The importance of reverse-recovery charge

A lesser understood parameter, reverse-recovery charge,  $Q_{rr}$ , is also known to make a large contribution to electro-magnetic emissions. During the dead-time in a motor-drive circuit, when both MOSFETs are turned off, free-wheel current flows briefly through the body diode of the low-side MOSFET: stored charge,  $Q_{rr}$ , accumulates across the body diode's PN junction, as shown in [Fig. 3](#).

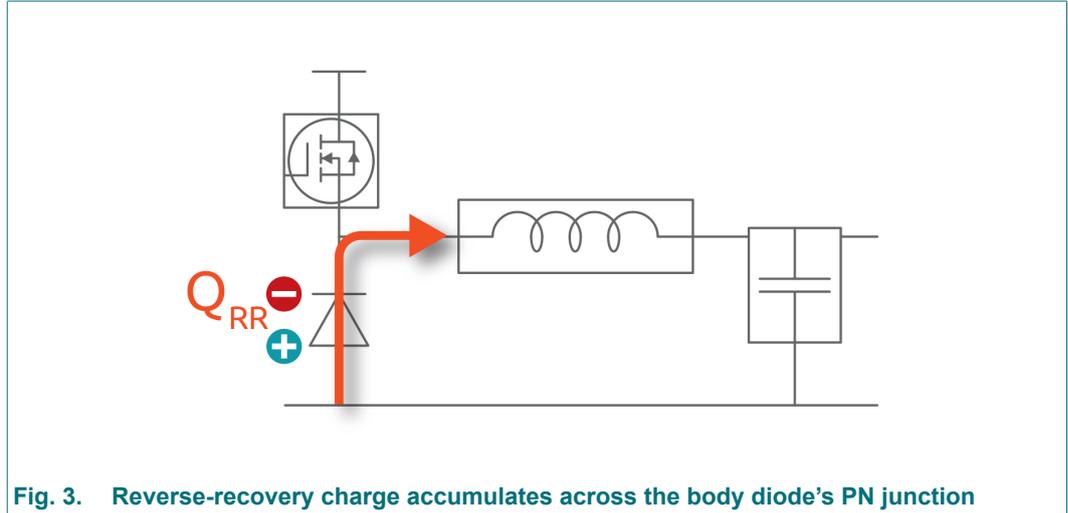

**Fig. 3. Reverse-recovery charge accumulates across the body diode's PN junction**

When the high-side MOSFET turns on, a current surge occurs, and flows briefly through the high-side and low-side MOSFETs, until the accumulated charge of the low-side is removed, as shown in [Fig. 4](#).  $I_{RM}$  (peak recovery current) can be relatively of high values and contributes to switching losses. This high-speed pulse also contributes markedly to electro-magnetic emissions.

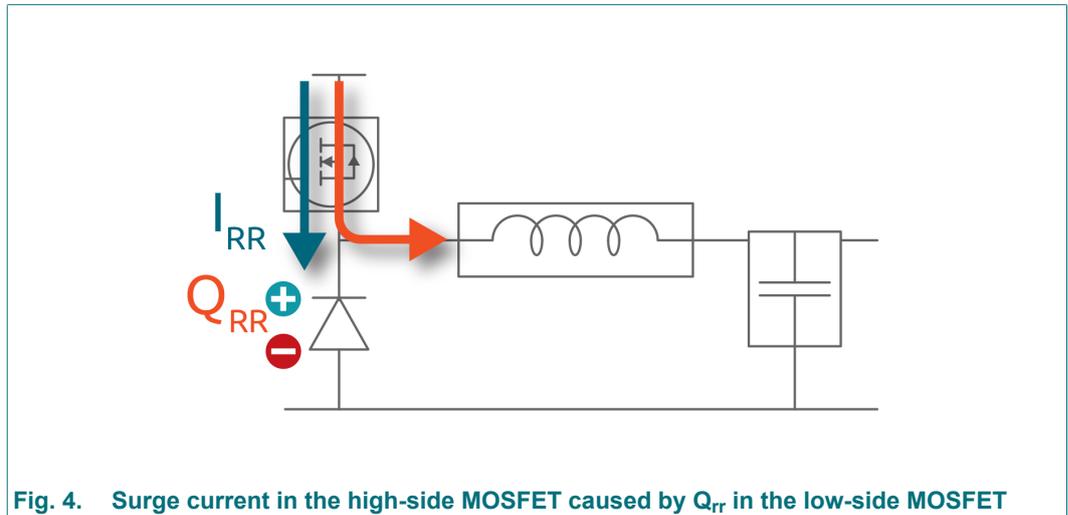

**Fig. 4. Surge current in the high-side MOSFET caused by  $Q_{rr}$  in the low-side MOSFET**

The  $Q_{rr}$  of a MOSFET: its importance in motor-control circuit designsLow  $Q_{rr}$  – reduced body diode reverse recovery current  $I_{rr}$ 

Fig. 5 shows the SPICE simulation results for 2 same devices, one of which was modelled to have twice the amount of  $Q_{rr}$ .

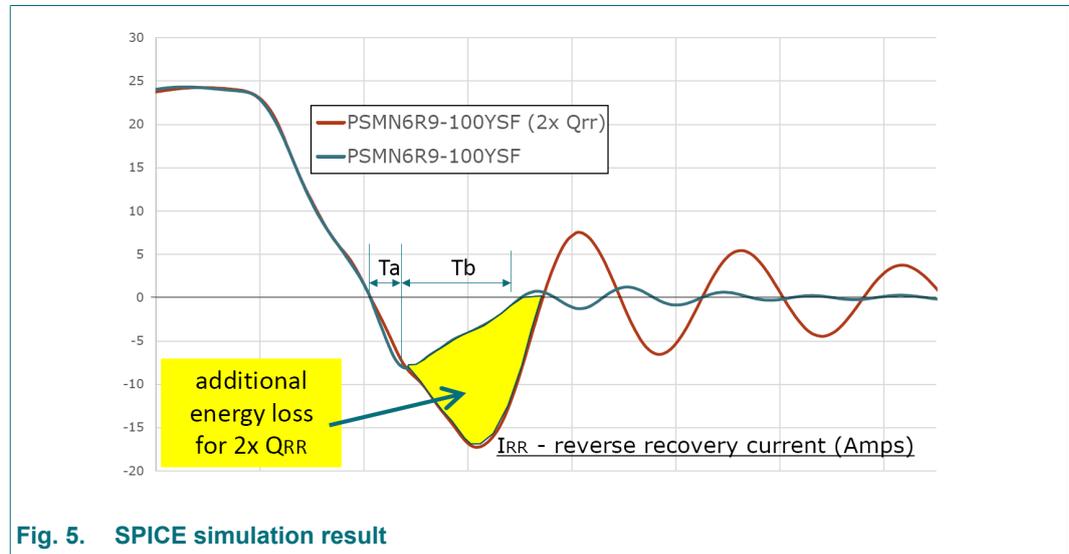


Fig. 5. SPICE simulation result

The SPICE simulations show the benefits of low  $Q_{rr}$  in switching applications,  $I_{rr}$  reduced by 50% for low  $Q_{rr}$  types. In Fig. 5 the shaded area represents the additional energy loss for parts with 2 x  $Q_{rr}$ .

Nexperia NextPower 100 V types have a higher softness factor ( $t_b / t_a > 1$ ) - gives lower ringing / resonance and lower spike voltage. Lower  $I_{rr}$ , ringing resonance also contributes to lower EMI emissions

## EMC

The  $I_{rr}$  pulse interacts with the MOSFET's lead-frame, and with the PCB's parasitic inductance and capacitance, to create a resonant circuit. The  $I_{rr}$  effect when combined with parasitic or package inductance will typically resonate at around 60 to 130 MHz.

Resonance can be reduced by carefully reducing the PCB's parasitic inductance through good PCB design, adding a snubber circuit, or by choosing MOSFETs with a low  $Q_{rr}$  rating.

The spectrum analyzer trace, shown in Fig. 6, compares the measured RF emissions for a low- $Q_{rr}$  NextPower 100 V MOSFET from Nexperia with those of a competitor's MOSFET the  $Q_{rr}$  of which is twice as high. In this example, the NextPower 100 V low- $Q_{rr}$  technology offers a reduction in electro-magnetic emissions of around 6 dB at frequencies between 70 MHz and 110 MHz. Use of the Nexperia low  $Q_{rr}$  part thus markedly reduces the risk of encountering EMC problems during qualification of a motor-drive design.

The Q<sub>rr</sub> of a MOSFET: its importance in motor-control circuit designs

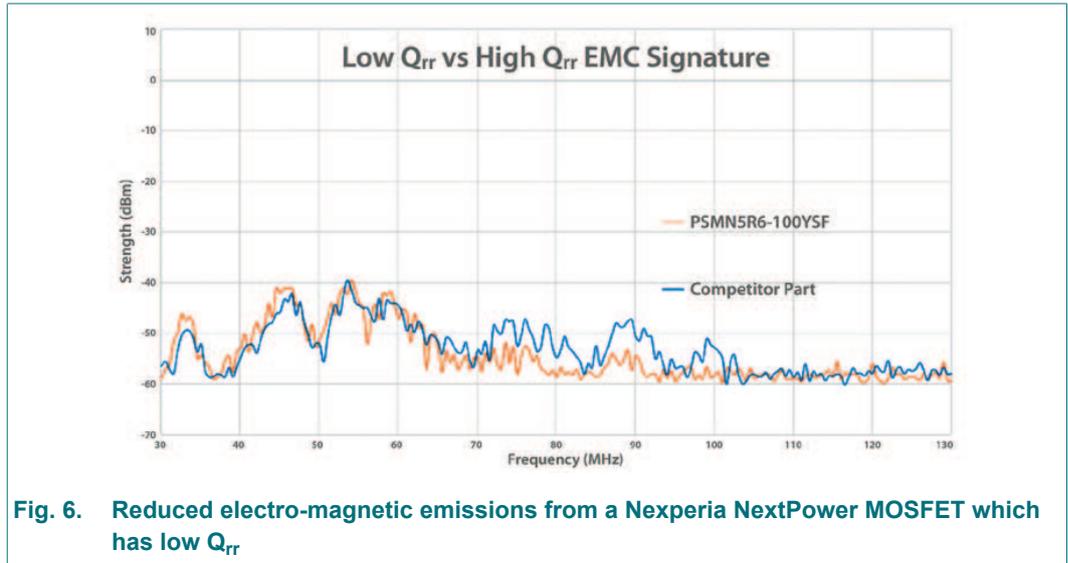


Fig. 6. Reduced electro-magnetic emissions from a Nexperia NextPower MOSFET which has low Q<sub>rr</sub>

### 4. Revision history

Table 1. Revision history

Revision number	Date	Description
1.0	2020-07-21	intitial version.

## 5. Legal information

### Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Nexperia does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, Nexperia does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Nexperia takes no responsibility for the content in this document if provided by an information source outside of Nexperia.

In no event shall Nexperia be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Nexperia's aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of Nexperia.

**Right to make changes** — Nexperia reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — Nexperia products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Nexperia product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Nexperia and its suppliers accept no liability for inclusion and/or use of Nexperia products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. Nexperia makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Nexperia products, and Nexperia accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Nexperia product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Nexperia does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Nexperia products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Nexperia does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

### Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

List of Tables

Table 1. Revision history.....5

### List of Figures

- Fig. 1. MOSFET temperature = 61.5 °C..... 2
- Fig. 2. MOSFET temperature = 65.6 °C..... 2
- Fig. 3. Reverse-recovery charge accumulates across the body diode's PN junction..... 3
- Fig. 4. Surge current in the high-side MOSFET caused by Qrr in the low-side MOSFET..... 3
- Fig. 5. SPICE simulation result..... 4
- Fig. 6. Reduced electro-magnetic emissions from a Nexperia NextPower MOSFET which has low Qrr.....5

## Contents

---

1. Introduction.....	2
2. Adding a gate resistor.....	2
3. The importance of reverse-recovery charge.....	3
4. Revision history.....	5
5. Legal information.....	6

---

© Nexperia B.V. 2020. All rights reserved

For more information, please visit: <http://www.nexperia.com>

For sales office addresses, please send an email to: [salesaddresses@nexperia.com](mailto:salesaddresses@nexperia.com)

Date of release: 21 July 2020

---